

Name: N.Divya Sai


Roll No.: FWC22094

ASSIGNMENT-1

0.1 Question-2007 Q43

0.4 Hardware

In the following circuit, X is given by

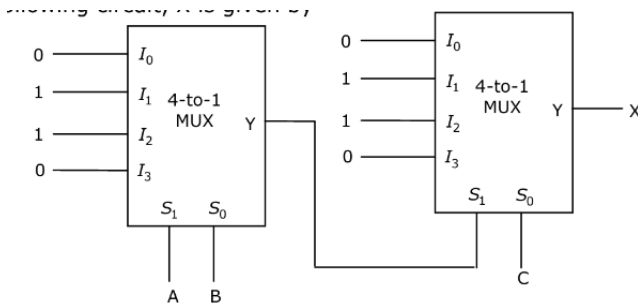

1. Pins 2,3,4 of Arduino are taken as input and pin 5 is taken as output.
2. Connect 5v and gnd to Breadbord. Connect Led and resistor on breadboard

0.5 Solution

Expression: $AB'C' + A'BC' + A'B'C + ABC$
Truth Table

0.2 Contents

Components	3
Hardware	4
Solution	5

A	0	0	0	0	1	1	1	1
B	0	0	1	1	0	0	1	1
C	0	1	0	1	0	1	0	1
X	0	1	1	0	1	0	0	1

Abstract- This manual shows the output X, for the given input A,B,C

1. Go to the working directory execute pio run and pio run -t upload.
2. Whenever you change the inputs you will see the respective output.

0.3 Components

Component	Value	Quantity
Resistor	220 Ohm	1
Arduino	UNO	1
Jumper Wires	M-M	6
Breadboard		1
LED		1

Codelink: <https://github.com/DivyaSai9621/FWC/blob/main/assignment-1/ide/codes/src/main.cpp>