

Name: N.Divya Sai

Roll No.: FWC22094

ASSIGNMENT-1

Avr-gcc

0.1 Question-2007 Q43

0.3 Components

| Component | Value | Quantity |
|-----------|-------|----------|
| Arduino | UNO | 1 |
| USB | | 1 |

0.4 Hardware

Connect arduino pins 2,3,4 to bread board. Based on the truth tabel, check for each value. Observe the in-built led on the arduino board will turn ON or OFF

0.5 Solution

Expression: $AB'C' + A'BC' + A'B'C + ABC$
Truth Table

| A | 0 | 0 | 0 | 0 | 1 | 1 | 1 | 1 |
|---|---|---|---|---|---|---|---|---|
| B | 0 | 0 | 1 | 1 | 0 | 0 | 1 | 1 |
| C | 0 | 1 | 0 | 1 | 0 | 1 | 0 | 1 |
| X | 0 | 1 | 1 | 0 | 1 | 0 | 0 | 1 |

0.2 Contents

| | |
|------------|---|
| Components | 3 |
| Hardware | 4 |
| Solution | 5 |

Abstract- This manual shows the output X, for the given input A,B,C

1. Go to the working directory and execute and upload the code.
2. Whenever you change the inputs you will see the respective output.