

Name: N.Divya Sai

Roll No.: FWC22094

ASSIGNMENT-1


Avr-gcc

0.1 Question-2007 Q43

0.3 Components

Component	Value	Quantity
Arduino	UNO	1
USB		1

In the following circuit,X is given by

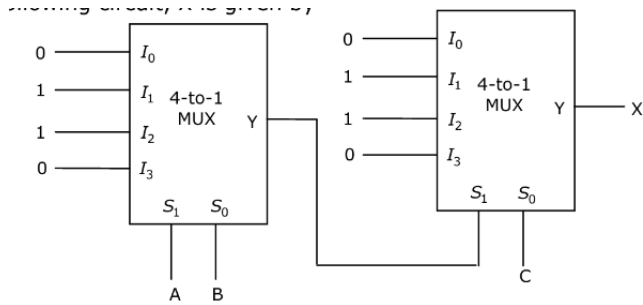

0.4 Hardware

Connect arduino pins 2,3,4 to bread board. Based on the truth tabel,check for each value. Observe the in-built led on the arduino board will turn ON or OFF

0.5 Solution

Expression: $AB'C' + A'BC' + A'B'C + ABC$

Truth Table

A	0	0	0	0	1	1	1	1
B	0	0	1	1	0	0	1	1
C	0	1	0	1	0	1	0	1
X	0	1	1	0	1	0	0	1

0.2 Contents

Components	3
Hardware	4
Solution	5

Abstract- This manual shows the output X,for the given input A,B,C

- 1.Go to the working directory and execute and upload the code.
- 2.Whenever you change the inputs you will see the respective output.